

<b>CE312</b>	<b>Report</b> <b>TP1 - Modulo 16, 4-bits Counter</b>
<b>Date:</b>	03/11/2020
<b>Students:</b>	CELLARD Rémi - Damien Pierson-Maury
<b>Subject:</b>	Modulo 16 Counter on 4-bits

## **1. Introduction**

In this report, we'll see how we can create a modulo 16 4-bits counter with VHDL code and simulate it in Vivado.

## **2. Code of the modulo 16 4-Bits counter component**

All the code for the component and the testbench are included at the end of the report, in annexes 1 and 2.

The chronogram of the testbench made by hand can be found in annex 3 and the chronogram resulting of the simulation in Vivado can be found in annex 4.

*Annex 1 - Modulo 16 counter component code*

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity compteur_16 is
port (
    clk : in STD_LOGIC; -- clock signal
    rst : in STD_LOGIC; -- reset signal
    enable : in STD_LOGIC; -- enable signal
    deb : out STD_LOGIC; -- bit overflow
    out_count : out STD_LOGIC_VECTOR (3 downto 0) -- counter signal
);
end entity;

architecture archcompteur of compteur_16 is
    signal debtmp : STD_LOGIC := '0';
    signal outtmp : STD_LOGIC_VECTOR (3 downto 0) := (others=>'0');
    -- two signal for made operations on it, because we can't on out an in signal
begin
    process(clk) -- active when event happen on signal clk
    begin
        if (clk'event and clk='1') then
            if rst='1' then
                debtmp <= '0';
                outtmp <= (others=>'0');
            elsif (enable='1') then -- no reset, counter enable
                if (outtmp = "1111") then -- add bit overflow + reset out_count
                    outtmp <= (others=>'0');
                    debtmp <= not debtmp;
                else
                    outtmp <= std_logic_vector(unsigned(outtmp)+ 1);
                    -- add 1 to unsigned
                end if;
            end if;
        end if;
    end process;

    -- output assignment
    deb <= debtmp;
    out_count <= outtmp;
end architecture;
```

*Annex 2 - Testbench code for the modulo 16 counter component*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity tb_compteur_16 is
end tb_compteur_16;


architecture tb of tb_compteur_16 is
    component compteur_16
        port (
            clk : in STD_LOGIC;
            rst : in STD_LOGIC;
            enable : in STD_LOGIC;
            deb : out STD_LOGIC; -- bit overflow
            out_count : out STD_LOGIC_VECTOR (3 downto 0)
        );
    end component;
    signal clk_tb, rst_tb, enable_tb, deb_tb : STD_LOGIC;
    signal out_count_tb : STD_LOGIC_VECTOR (3 downto 0);
    begin
        compteur: compteur_16 port map (clk=>clk_tb, rst=>rst_tb, enable=>enable_tb, deb=>deb_tb,
out_count=>out_count_tb);

        clock_10mhz_generation : process -- simulation of the clock signal
            begin
                clk_tb <= '0';
                wait for 50 ns;
                clk_tb <= '1';
                wait for 50 ns;
            end process;

        proreset: process -- simulation of the reset signal
            begin
                rst_tb <= '1';
                wait for 100 ns; -- we maintain the rst_tb signal on 100 ns
                rst_tb <= '0';
                wait for 1000 ns; -- we maintain the rst_tb signal on 100 ns
                rst_tb <= '1';
                wait for 100 ns; -- we maintain the rst_tb signal on 100 ns
                rst_tb <= '0';
                wait; -- we remove it permanently
            end process;

        procenable: process -- simulation of the enable signal
            begin
                enable_tb <= '1';
                wait for 325 ns;
                enable_tb <= '0';
                wait for 75 ns;
                enable_tb <= '1';
                wait;
            end process;
        end architecture;
```

Annex 3 - Hand-processed chronogram of the testbench

 

Annex 4 - Vivado-processed chronogram of the testbench, after simulation

